

L.I.S.T. Group

LONG ISLAND
SINCLAIR TIMEX
GROUP

Hello DON!
HERE'S A SAMPLER
OF OUR NEWSLETTER.

1985

LIST
P.O. BOX 438
Centerport, N.Y. 11721-438

Dear Inquirer:

The LIST GROUP has been formed to help keep the spirit of the Sinclair-Timex "peoples" computer alive. At this point, we're getting organized; officers have been elected and a monthly newsletter started. A Charter is yet to be written, but "meetings" are held once per month, usually in member's homes.


Despite the lack of a written charter the general goals of our group include:

- 1) Exchange of information, ideas and knowledge on and about TS computers.
- 2) Hardware and Software demonstration and perhaps even exchange.
- 3) Community service to increase computer literacy.
- 4) Perhaps some advantage to members through the exercise of group buying power.

Right now we have about 60 members and a modest budget. A circulating tape library has begun, and we have generated a pretty substantial newsletter, a few sample pages of which are attached. See the newsletter pages for membership/subscription information.

Write to us and tell us what you'd like to see in the newsletter and/or send us some of your work to share with other members. Special Interest Groups - TS 1000 and TS 2008/Spectrum, will soon be forming.

Hope to hear from you soon.

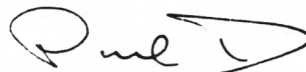

Paul Donnelly
Sec'y Treas.

LISTing Policy:

Annual Dues.....\$15.00 Issue Price \$1.50 (includes P&P)

One "Sample" copy sent upon receipt of large SASE.

Copies provided on exchange basis with other bona fide user groups.

L.I.S.T.ing is published monthly by LIST (Long Island Sinclair Timex) Group
a not-for-profit users group

Your reviews, programs, comments, hardware projects, etc., are eagerly solicited for publication in LISTing.

@Copyright 1984, LIST Group. No portion of this publication may be reproduced, in any form, without the express written consent of LIST or the original author.

Please note our new address - P.O. BOX 438, Centerport, N.Y. 11721-0438
Mail sent to the old address must be forwarded there and will take longer to reach us.

NOTE: PARTIAL YEAR MEMBERSHIPS AVAILABLE

Normal membership year is Feb. through Jan. at cost of \$15.00.(U.S.)
By keeping as many members as possible on that basis, we keep our costs and chances of error down.

If you wish to begin subscribing later in the year, please sign up for the end of this year and all of next.

We will accept partial years or different subscription runs, on a limited basis (particularly from members outside the U.S.)
But, please be aware that, addition to possible rate increases, your "account" must be handled "by hand" and errors may occur.
International (EX Canada) subscribers will receive as many issues as we can afford to mail.

CLASSIFIED ADS

Got something to sell or trade? Members get a free one time insertion of up to 50 words. 10¢/word-otherwise (your photo ready copy); 15¢/word-we compose.

SPECTRUM ROMs - \$19.95 (18.00 for List members) includes P & P. LIST Associates, 10 Idle Day Drive, Centerport, N.Y. 11721.

DK'Tronics Light Pen (for Spectrum - works on 2068 buss) \$35.00 (includes P & P) LIST Associates, 10 Idle Day Drive, Centerport, N.Y. 11721.

A NOTE ON: LIST ASSOCIATES
LISTA is a cooperative buying service. It is not an official organ of LIST Group.

=====

LONG ISLAND SINCLAIR TIMEX GROUP (L.I.S.T.) supports ZX81, TS 1000 and TS 2068 computers. Annual dues \$15. - includes a monthly newsletter and library program cassettes. Sample newsletter on request. Include a large S.A.S.E. with 37 cents postage. Spectrum ROMs for sale \$19.95 includes P&P. L.I.S.T. PO Box 438 Centerport, NY 11721-0438

POLICY ON CONTRIBUTED MATERIAL:

We are always looking for interesting articles, programs, reviews etc. to help keep our members informed and entertained. Articles submitted for publication are printed on the following basis:

1. You the writer, maintain the full copyright and can resell, lend or give away your work, as you wish.
2. We are granted the right to publish your material, in the original issue in which it appears. Reprints (e.g., to supply orders for back issues) will include your material as a part of its original issue. We are not allowed to sell your material in any other way, without your express written consent;

We can't (for now) pay you for your material, but you will receive a copy of the issue in which it is published, even if you're not a member. You may get more than one issue and you will definitely earn the respect and appreciation by your grateful peers.

If you have a program or article about something you've tried, please send it in. Our group interests are so varied that I can almost certainly guarantee that someone else can use your expertise to solve his problem.

February 1985

I.	Meeting Notes	1
II.	Policy, Classified - Index	2
III.	Members Software/Articles	
	Clock: S. Livingston	3
	Tas man Utilities & Lister	
	A. Cunningham	4
	Using The TS1000 in Education	
	S. Kaye	5
	TS1000 Header Reader	
	C. Barut	6
	Spectrum Computing - Review	
	P. Donnelly	7
IV.	Technical Report	
	Power Supplies	8
	J. Peeler	
	2068 Outport (Part 2)	9
	R. Gilder	
	Hackers Notebook	10
	Joysticks	
	TS2068/Spectrum Microdrive	11
	R. Pershy	
	N. Pashtoon	
	Sears RGB Monitor - Review	12
	P. Donnelly	
V.	Graphics	
	Curves - P. Bingham	13
	Program Samples	14
VI.	Communication/WP	
	Tasword II - mini review	15
	P. Donnelly	
	BASICODE	15
VII.	Letters to List	16,17,18
VIII.	Vendor Report	19
IX.	Special Features	20
	ROM Atlas - Part II	
	N. Pashtoon	
	B. Microdrive SAGA Continues	21,22
	N. Pashtoon	
X.	Members Only	23
	Map to February Meeting	

TIMEX-SINCLAIR Software/Hardware
(2068-1000 ***** SPECTRUM-1000)
* SMART II Modem software...\$23.88
* ROMSWITCH for 2068 - lets your 2068 run SPECTRUM programs \$49.88
* 2068 PINBALL CARTRIDGE...\$19.95
* VU-FILE/VU-CALC/VU-3D-ea.\$15.95
* Many SPECTRUM Titles below \$20.
* 2068 MICRO-DRIVE SYSTEM.\$189.88
* Send a 2 stamp LSASE for our complete catalog !!
*** SUM-WARE ***
810 Mammoth ALDEN NY 14004

2-83

ADAPTING THE TI KEYBOARD TO THE TS1000

This article is for those lucky people who have delayed, hesitated or just have not gotten around to wiring up their "big" keyboards.

In the last few months Texas Instruments has dumped on the surplus market a huge quantity of new components designed for use with the now defunct TI 99/4, including power supplies, RF modulators and TMS 9918 chips. One of the prize finds from this lot is the 48 key keyboard which can be purchased from numerous vendors; prices range from \$3 to \$10 (a list of vendors is provided for you at the end of the article).

The hardware of the TS keyboard system is quite straightforward. It consists of 40 normally open switches and eight diodes arranged in a matrix pattern. The status of the switches is periodically read by the ROM by an IM instruction to port FEH. These details, however, are not of concern in wiring up your keyboard; the object of the task is to duplicate the wiring of the membrane pads.

Preparing the Keyboard

The steps involved in transforming your keyboard from TI to TS follow. The instructions are the same for the grey or the black keyboard; they are functionally the same. Do note, however, that the keytops are not interchangeable as their slopes are different. You can also do this project by rerouting traces on the PC board (by cutting and jumpering), but this method can put you in a foul temper in very short order. I chose to start with a clean slate by eliminating all the traces.

Desolder all key contacts (2 Each) on the PC. This job is made easier with a vacuum type desoldering gun from Radio Shack (\$6.95). Desolder and store the very important cable connector TI provides; you will need it later. Carefully pry the PC board off the keys. It will separate cleanly with a little urging. Never mind that lots of little washers have also fallen under the workbench, lost for posterity, you will not need them. The next step is to grind off all the foil and the green protective layer leaving a naked epoxy board ready to hardware to your specifications. Note that the method of attack for this job is dictated by the technology available to you and/or how hard you like to work at things. I used a grinder with a 6 inch wheel passing the board in front of the small cutting surface many, many times. My thought during this process was how much easier this would be with a belt sander. Once the board is stripped you can be proud of yourself for having reversed the work of mighty TI for use on your humble ZX. Don't stare at it too long; the main part of the conversion is yet to come.

Wiring Your Keyboard

First decide where you will locate the mechanical shift lock key. This will not be possible once wiring is underway. I used 30AWG wire wrap wire successfully for the whole project. I suggest you get as many colors as you can afford. FIG 1. is a diagram from the MULE Electronics Keyboard Symbol Kit. The diagram shows all

necessary connections. You can daisy chain rows or columns if you use bare wire. This saves a considerable amount of time over cutting small lengths of wire as you will have to for the rest of the project. Once the matrix is wired, you are ready for your bonus; shifted function special purpose keys. The rule to remember in wiring these is to evaluate the shortest route to a particular Address or KB line, before you take soldering gun in hand. It's beyond the scope of this article to detail the methods used to obtain shifted functions or repeat keys. Articles in Sync, Syntax and TS Horizons have covered these topics. The MULE kit also covers the subject thoroughly, providing diagrams on how to obtain all of the shifted functions. This is one area where you can customize your computer to put it into a category by itself. I have wired 4 special purpose keys and find that I use them constantly to increase the utility of data base and word processing programs.

Connecting Your KB to the Computer

There is no easy single way to bring keyboard and Address lines from your new keyboard to the computer chassis. The connector provided (remember I asked you to save it) by TI has 15 slots; it is a press-on type of connector. Standard ribbon cable can be push fitted into these slots with the help of a screwdriver. Once this is done you have a connector with a long stretch of ribbon cable. How do you get this secured to your newly rewired keyboard? One way is to epoxy a strip of a single in-line IC spacing header to the KB and to solder your cable/connector assembly to this (See Fig.3) The header material can be bought in a strip and cut to the 15 position size to fit into predrilled holes already there. Radio Shack no longer carries this material but it can be bought from a variety of other sources.

Now, on to the last bit of wiring; To finish the project you must bring your KB and Address lines to your new header. The thing to remember here is that your 5 KB lines will be on the left and your 8 ADD lines will be on your right on the finished project. If you are going to retain the keyboard connectors on your computer chassis you will have to make a one sided .1 spacing edge connector to fit into the TS keyboard connectors (See FIG 2.). You can use the Zebra C112 45 pos male card edge connector (\$2.50) cut down to size (8 and 5 slot) and with the back traces buffed off to fit into the KB connector slots. Of course the other alternative is to directly wire the keyboard to the chassis.


The last part of the project is to install your new keytops from the MULE kit. These high quality plastic symbol tops go on easily, look professional and seem to last forever. Comprehensive instructions are enclosed with the product. The symbols on the sides of the TI keys can be sanded off easily with 500 grit while you are doing your keytops.

By now you are either totally confused or the proud owner of a newly converted TS/TI keyboard. For the adventurous few who absolutely demand a numeric keypad, this too is possible. You must buy a second keyboard to scavenge the keys. If you would like to do this project, send S.S.R.E. and I will send you a drilling template and wiring diagram.

3-85-

Don Barut

FIG1.

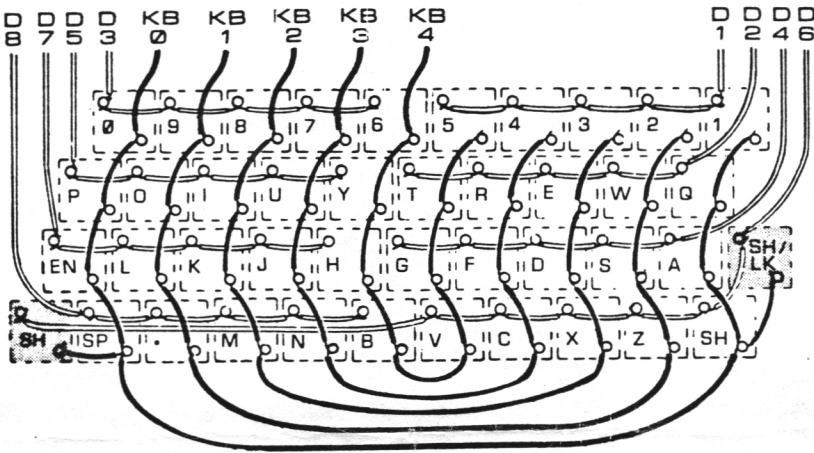

WIRING OF KEY-SWITCH TERMINALS (BOTTOM VIEW)

Mule Electronics
Dept. 310
444 Lincoln Blvd.
Venice CA 90291
213-452-1205
TS1000 KB Conv. Kit - \$11.95
Shifted Fn. Set - \$5.00

Source of TI KBs
Radio Shack
Anywhere USA
Check availability



Arnold Co. (TX)
214-576-229
\$5.95

American Design Components (NJ)
201-939-2710
\$5.95

Saket Elect. (TX)
214-234-8832
\$3.50

Lolin Elect. (TX)
214-234-8832
\$3.50

FIG2.

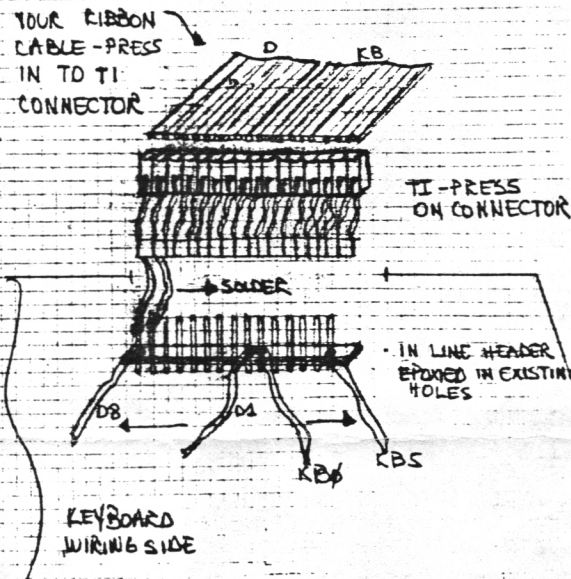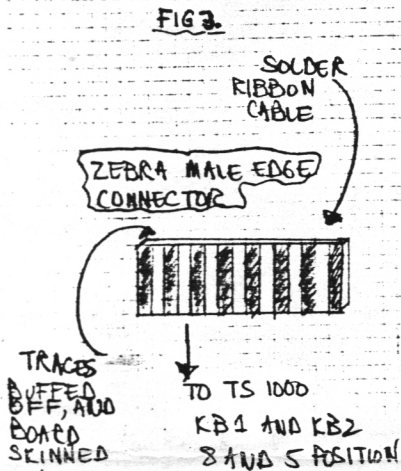

List
Group

3-85

```


100 REM ROBOT
110 CLS
120 PRINT AT 4,2;"HERE ARE YOUR
CONTROLS KEYS:"
130 PRINT AT 3,13;"U I O"
140 PRINT AT 7,13;"J L"
150 PRINT AT 0,13;"N M."
160 PRINT AT 1,0;"PRESS<ENTER>T
0 CONTINUE"
170 LET K#=INKEY#
180 IF K#<>CHR# 118 THEN GOTO 7
0
190 CLS
200 PRINT
210 LET SC=PEEK 16396+256*PEEK
220 LET S=1000
230 LET IB=100
240 LET IO=100
250 LET IJ=0
260 LET IL=0
270 LET IM=0
280 LET IN=0
290 LET IP=0
300 LET IS=0
310 LET IT=0
320 LET IU=0
330 LET IV=0
340 LET IW=0
350 LET IX=0
360 LET IY=0
370 LET IZ=0
380 LET IA=0
390 LET IB=0
400 LET IC=0
410 LET ID=0
420 LET IE=0
430 LET IF=0
440 LET IG=0
450 LET IH=0
460 LET II=0
470 LET IJ=0
480 LET IK=0
490 LET IL=0
500 LET IM=0
510 LET IN=0
520 LET IO=0
530 LET IP=0
540 LET IQ=0
550 LET IR=0
560 LET IS=0
570 LET IT=0
580 LET IU=0
590 LET IV=0
600 LET IW=0
610 LET IX=0
620 LET IY=0
630 LET IZ=0
640 LET IA=0
650 LET IB=0
660 LET IC=0
670 LET ID=0
680 LET IE=0
690 LET IF=0
700 LET IG=0
710 LET IH=0
720 LET II=0
730 LET IJ=0
740 LET IK=0
750 LET IL=0
760 LET IM=0
770 LET IN=0
780 LET IO=0
790 LET IP=0
800 LET IQ=0
810 LET IR=0
820 LET IS=0
830 LET IT=0
840 LET IU=0
850 LET IV=0
860 LET IW=0
870 LET IX=0
880 LET IY=0
890 LET IZ=0
900 LET IA=0
910 LET IB=0
920 LET IC=0
930 LET ID=0
940 LET IE=0
950 LET IF=0
960 LET IG=0
970 LET IH=0
980 LET II=0
990 LET IJ=0
1000 LET IK=0
1010 LET IL=0
1020 LET IM=0
1030 LET IN=0
1040 LET IO=0
1050 LET IP=0
1060 LET IQ=0
1070 LET IR=0
1080 LET IS=0
1090 LET IT=0
1100 LET IU=0
1110 LET IV=0
1120 LET IW=0
1130 LET IX=0
1140 LET IY=0
1150 LET IZ=0
1160 LET IA=0
1170 LET IB=0
1180 LET IC=0
1190 LET ID=0
1200 LET IE=0
1210 LET IF=0
1220 LET IG=0
1230 LET IH=0
1240 LET II=0
1250 LET IJ=0
1260 LET IK=0
1270 LET IL=0
1280 LET IM=0
1290 LET IN=0
1300 LET IO=0
1310 LET IP=0
1320 LET IQ=0
1330 LET IR=0
1340 LET IS=0
1350 LET IT=0
1360 LET IU=0
1370 LET IV=0
1380 LET IW=0
1390 LET IX=0
1400 LET IY=0
1410 LET IZ=0
1420 LET IA=0
1430 LET IB=0
1440 LET IC=0
1450 LET ID=0
1460 LET IE=0
1470 LET IF=0
1480 LET IG=0
1490 LET IH=0
1500 LET II=0
1510 LET IJ=0
1520 LET IK=0
1530 LET IL=0
1540 LET IM=0
1550 LET IN=0
1560 LET IO=0
1570 LET IP=0
1580 LET IQ=0
1590 LET IR=0
1600 LET IS=0
1610 LET IT=0
1620 LET IU=0
1630 LET IV=0
1640 LET IW=0
1650 LET IX=0
1660 LET IY=0
1670 LET IZ=0
1680 LET IA=0
1690 LET IB=0
1700 LET IC=0
1710 LET ID=0
1720 LET IE=0
1730 LET IF=0
1740 LET IG=0
1750 LET IH=0
1760 LET II=0
1770 LET IJ=0
1780 LET IK=0
1790 LET IL=0
1800 LET IM=0
1810 LET IN=0
1820 LET IO=0
1830 LET IP=0
1840 LET IQ=0
1850 LET IR=0
1860 LET IS=0
1870 LET IT=0
1880 LET IU=0
1890 LET IV=0
1900 LET IW=0
1910 LET IX=0
1920 LET IY=0
1930 LET IZ=0
1940 LET IA=0
1950 LET IB=0
1960 LET IC=0
1970 LET ID=0
1980 LET IE=0
1990 LET IF=0
2000 LET IG=0
2010 LET IH=0
2020 LET II=0
2030 LET IJ=0
2040 LET IK=0
2050 LET IL=0
2060 LET IM=0
2070 LET IN=0
2080 LET IO=0
2090 LET IP=0
2100 LET IQ=0
2110 LET IR=0
2120 LET IS=0
2130 LET IT=0
2140 LET IU=0
2150 LET IV=0
2160 LET IW=0
2170 LET IX=0
2180 LET IY=0
2190 LET IZ=0
2200 LET IA=0
2210 LET IB=0
2220 LET IC=0
2230 LET ID=0
2240 LET IE=0
2250 LET IF=0
2260 LET IG=0
2270 LET IH=0
2280 LET II=0
2290 LET IJ=0
2300 LET IK=0
2310 LET IL=0
2320 LET IM=0
2330 LET IN=0
2340 LET IO=0
2350 LET IP=0
2360 LET IQ=0
2370 LET IR=0
2380 LET IS=0
2390 LET IT=0
2400 LET IU=0
2410 LET IV=0
2420 LET IW=0
2430 LET IX=0
2440 LET IY=0
2450 LET IZ=0
2460 LET IA=0
2470 LET IB=0
2480 LET IC=0
2490 LET ID=0
2500 LET IE=0
2510 LET IF=0
2520 LET IG=0
2530 LET IH=0
2540 LET II=0
2550 LET IJ=0
2560 LET IK=0
2570 LET IL=0
2580 LET IM=0
2590 LET IN=0
2600 LET IO=0
2610 LET IP=0
2620 LET IQ=0
2630 LET IR=0
2640 LET IS=0
2650 LET IT=0
2660 LET IU=0
2670 LET IV=0
2680 LET IW=0
2690 LET IX=0
2700 LET IY=0
2710 LET IZ=0
2720 LET IA=0
2730 LET IB=0
2740 LET IC=0
2750 LET ID=0
2760 LET IE=0
2770 LET IF=0
2780 LET IG=0
2790 LET IH=0
2800 LET II=0
2810 LET IJ=0
2820 LET IK=0
2830 LET IL=0
2840 LET IM=0
2850 LET IN=0
2860 LET IO=0
2870 LET IP=0
2880 LET IQ=0
2890 LET IR=0
2900 LET IS=0
2910 LET IT=0
2920 LET IU=0
2930 LET IV=0
2940 LET IW=0
2950 LET IX=0
2960 LET IY=0
2970 LET IZ=0
2980 LET IA=0
2990 LET IB=0
3000 LET IC=0
3010 LET ID=0
3020 LET IE=0
3030 LET IF=0
3040 LET IG=0
3050 LET IH=0
3060 LET II=0
3070 LET IJ=0
3080 LET IK=0
3090 LET IL=0
3100 LET IM=0
3110 LET IN=0
3120 LET IO=0
3130 LET IP=0
3140 LET IQ=0
3150 LET IR=0
3160 LET IS=0
3170 LET IT=0
3180 LET IU=0
3190 LET IV=0
3200 LET IW=0
3210 LET IX=0
3220 LET IY=0
3230 LET IZ=0
3240 LET IA=0
3250 LET IB=0
3260 LET IC=0
3270 LET ID=0
3280 LET IE=0
3290 LET IF=0
3300 LET IG=0
3310 LET IH=0
3320 LET II=0
3330 LET IJ=0
3340 LET IK=0
3350 LET IL=0
3360 LET IM=0
3370 LET IN=0
3380 LET IO=0
3390 LET IP=0
3400 LET IQ=0
3410 LET IR=0
3420 LET IS=0
3430 LET IT=0
3440 LET IU=0
3450 LET IV=0
3460 LET IW=0
3470 LET IX=0
3480 LET IY=0
3490 LET IZ=0
3500 LET IA=0
3510 LET IB=0
3520 LET IC=0
3530 LET ID=0
3540 LET IE=0
3550 LET IF=0
3560 LET IG=0
3570 LET IH=0
3580 LET II=0
3590 LET IJ=0
3600 LET IK=0
3610 LET IL=0
3620 LET IM=0
3630 LET IN=0
3640 LET IO=0
3650 LET IP=0
3660 LET IQ=0
3670 LET IR=0
3680 LET IS=0
3690 LET IT=0
3700 LET IU=0
3710 LET IV=0
3720 LET IW=0
3730 LET IX=0
3740 LET IY=0
3750 LET IZ=0
3760 LET IA=0
3770 LET IB=0
3780 LET IC=0
3790 LET ID=0
3800 LET IE=0
3810 LET IF=0
3820 LET IG=0
3830 LET IH=0
3840 LET II=0
3850 LET IJ=0
3860 LET IK=0
3870 LET IL=0
3880 LET IM=0
3890 LET IN=0
3900 LET IO=0
3910 LET IP=0
3920 LET IQ=0
3930 LET IR=0
3940 LET IS=0
3950 LET IT=0
3960 LET IU=0
3970 LET IV=0
3980 LET IW=0
3990 LET IX=0
4000 LET IY=0
4010 LET IZ=0
4020 LET IA=0
4030 LET IB=0
4040 LET IC=0
4050 LET ID=0
4060 LET IE=0
4070 LET IF=0
4080 LET IG=0
4090 LET IH=0
4100 LET II=0
4110 LET IJ=0
4120 LET IK=0
4130 LET IL=0
4140 LET IM=0
4150 LET IN=0
4160 LET IO=0
4170 LET IP=0
4180 LET IQ=0
4190 LET IR=0
4200 LET IS=0
4210 LET IT=0
4220 LET IU=0
4230 LET IV=0
4240 LET IW=0
4250 LET IX=0
4260 LET IY=0
4270 LET IZ=0
4280 LET IA=0
4290 LET IB=0
4300 LET IC=0
4310 LET ID=0
4320 LET IE=0
4330 LET IF=0
4340 LET IG=0
4350 LET IH=0
4360 LET II=0
4370 LET IJ=0
4380 LET IK=0
4390 LET IL=0
4400 LET IM=0
4410 LET IN=0
4420 LET IO=0
4430 LET IP=0
4440 LET IQ=0
4450 LET IR=0
4460 LET IS=0
4470 LET IT=0
4480 LET IU=0
4490 LET IV=0
4500 LET IW=0
4510 LET IX=0
4520 LET IY=0
4530 LET IZ=0
4540 LET IA=0
4550 LET IB=0
4560 LET IC=0
4570 LET ID=0
4580 LET IE=0
4590 LET IF=0
4600 LET IG=0
4610 LET IH=0
4620 LET II=0
4630 LET IJ=0
4640 LET IK=0
4650 LET IL=0
4660 LET IM=0
4670 LET IN=0
4680 LET IO=0
4690 LET IP=0
4700 LET IQ=0
4710 LET IR=0
4720 LET IS=0
4730 LET IT=0
4740 LET IU=0
4750 LET IV=0
4760 LET IW=0
4770 LET IX=0
4780 LET IY=0
4790 LET IZ=0
4800 LET IA=0
4810 LET IB=0
4820 LET IC=0
4830 LET ID=0
4840 LET IE=0
4850 LET IF=0
4860 LET IG=0
4870 LET IH=0
4880 LET II=0
4890 LET IJ=0
4900 LET IK=0
4910 LET IL=0
4920 LET IM=0
4930 LET IN=0
4940 LET IO=0
4950 LET IP=0
4960 LET IQ=0
4970 LET IR=0
4980 LET IS=0
4990 LET IT=0
5000 LET IU=0
5010 LET IV=0
5020 LET IW=0
5030 LET IX=0
5040 LET IY=0
5050 LET IZ=0
5060 LET IA=0
5070 LET IB=0
5080 LET IC=0
5090 LET ID=0
5100 LET IE=0
5110 LET IF=0
5120 LET IG=0
5130 LET IH=0
5140 LET II=0
5150 LET IJ=0
5160 LET IK=0
5170 LET IL=0
5180 LET IM=0
5190 LET IN=0
5200 LET IO=0
5210 LET IP=0
5220 LET IQ=0
5230 LET IR=0
5240 LET IS=0
5250 LET IT=0
5260 LET IU=0
5270 LET IV=0
5280 LET IW=0
5290 LET IX=0
5300 LET IY=0
5310 LET IZ=0
5320 LET IA=0
5330 LET IB=0
5340 LET IC=0
5350 LET ID=0
5360 LET IE=0
5370 LET IF=0
5380 LET IG=0
5390 LET IH=0
5400 LET II=0
5410 LET IJ=0
5420 LET IK=0
5430 LET IL=0
5440 LET IM=0
5450 LET IN=0
5460 LET IO=0
5470 LET IP=0
5480 LET IQ=0
5490 LET IR=0
5500 LET IS=0
5510 LET IT=0
5520 LET IU=0
5530 LET IV=0
5540 LET IW=0
5550 LET IX=0
5560 LET IY=0
5570 LET IZ=0
5580 LET IA=0
5590 LET IB=0
5600 LET IC=0
5610 LET ID=0
5620 LET IE=0
5630 LET IF=0
5640 LET IG=0
5650 LET IH=0
5660 LET II=0
5670 LET IJ=0
5680 LET IK=0
5690 LET IL=0
5700 LET IM=0
5710 LET IN=0
5720 LET IO=0
5730 LET IP=0
5740 LET IQ=0
5750 LET IR=0
5760 LET IS=0
5770 LET IT=0
5780 LET IU=0
5790 LET IV=0
5800 LET IW=0
5810 LET IX=0
5820 LET IY=0
5830 LET IZ=0
5840 LET IA=0
5850 LET IB=0
5860 LET IC=0
5870 LET ID=0
5880 LET IE=0
5890 LET IF=0
5900 LET IG=0
5910 LET IH=0
5920 LET II=0
5930 LET IJ=0
5940 LET IK=0
5950 LET IL=0
5960 LET IM=0
5970 LET IN=0
5980 LET IO=0
5990 LET IP=0
6000 LET IQ=0
6010 LET IR=0
6020 LET IS=0
6030 LET IT=0
6040 LET IU=0
6050 LET IV=0
6060 LET IW=0
6070 LET IX=0
6080 LET IY=0
6090 LET IZ=0
6100 LET IA=0
6110 LET IB=0
6120 LET IC=0
6130 LET ID=0
6140 LET IE=0
6150 LET IF=0
6160 LET IG=0
6170 LET IH=0
6180 LET II=0
6190 LET IJ=0
6200 LET IK=0
6210 LET IL=0
6220 LET IM=0
6230 LET IN=0
6240 LET IO=0
6250 LET IP=0
6260 LET IQ=0
6270 LET IR=0
6280 LET IS=0
6290 LET IT=0
6300 LET IU=0
6310 LET IV=0
6320 LET IW=0
6330 LET IX=0
6340 LET IY=0
6350 LET IZ=0
6360 LET IA=0
6370 LET IB=0
6380 LET IC=0
6390 LET ID=0
6400 LET IE=0
6410 LET IF=0
6420 LET IG=0
6430 LET IH=0
6440 LET II=0
6450 LET IJ=0
6460 LET IK=0
6470 LET IL=0
6480 LET IM=0
6490 LET IN=0
6500 LET IO=0
6510 LET IP=0
6520 LET IQ=0
6530 LET IR=0
6540 LET IS=0
6550 LET IT=0
6560 LET IU=0
6570 LET IV=0
6580 LET IW=0
6590 LET IX=0
6600 LET IY=0
6610 LET IZ=0
6620 LET IA=0
6630 LET IB=0
6640 LET IC=0
6650 LET ID=0
6660 LET IE=0
6670 LET IF=0
6680 LET IG=0
6690 LET IH=0
6700 LET II=0
6710 LET IJ=0
6720 LET IK=0
6730 LET IL=0
6740 LET IM=0
6750 LET IN=0
6760 LET IO=0
6770 LET IP=0
6780 LET IQ=0
6790 LET IR=0
6800 LET IS=0
6810 LET IT=0
6820 LET IU=0
6830 LET IV=0
6840 LET IW=0
6850 LET IX=0
6860 LET IY=0
6870 LET IZ=0
6880 LET IA=0
6890 LET IB=0
6900 LET IC=0
6910 LET ID=0
6920 LET IE=0
6930 LET IF=0
6940 LET IG=0
6950 LET IH=0
6960 LET II=0
6970 LET IJ=0
6980 LET IK=0
6990 LET IL=0
7000 LET IM=0
7010 LET IN=0
7020 LET IO=0
7030 LET IP=0
7040 LET IQ=0
7050 LET IR=0
7060 LET IS=0
7070 LET IT=0
7080 LET IU=0
7090 LET IV=0
7100 LET IW=0
7110 LET IX=0
7120 LET IY=0
7130 LET IZ=0
7140 LET IA=0
7150 LET IB=0
7160 LET IC=0
7170 LET ID=0
7180 LET IE=0
7190 LET IF=0
7200 LET IG=0
7210 LET IH=0
7220 LET II=0
7230 LET IJ=0
7240 LET IK=0
7250 LET IL=0
7260 LET IM=0
7270 LET IN=0
7280 LET IO=0
7290 LET IP=0
7300 LET IQ=0
7310 LET IR=0
7320 LET IS=0
7330 LET IT=0
7340 LET IU=0
7350 LET IV=0
7360 LET IW=0
7370 LET IX=0
7380 LET IY=0
7390 LET IZ=0
7400 LET IA=0
7410 LET IB=0
7420 LET IC=0
7430 LET ID=0
7440 LET IE=0
7450 LET IF=0
7460 LET IG=0
7470 LET IH=0
7480 LET II=0
7490 LET IJ=0
7500 LET IK=0
7510 LET IL=0
7520 LET IM=0
7530 LET IN=0
7540 LET IO=0
7550 LET IP=0
7560 LET IQ=0
7570 LET IR=0
7580 LET IS=0
7590 LET IT=0
7600 LET IU=0
7610 LET IV=0
7620 LET IW=0
7630 LET IX=0
7640 LET IY=0
7650 LET IZ=0
7660 LET IA=0
7670 LET IB=0
7680 LET IC=0
7690 LET ID=0
7700 LET IE=0
7710 LET IF=0
7720 LET IG=0
7730 LET IH=0
7740 LET II=0
7750 LET IJ=0
7760 LET IK=0
7770 LET IL=0
7780 LET IM=0
7790 LET IN=0
7800 LET IO=0
7810 LET IP=0
7820 LET IQ=0
7830 LET IR=0
7840 LET IS=0
7850 LET IT=0
7860 LET IU=0
7870 LET IV=0
7880 LET IW=0
7890 LET IX=0
7900 LET IY=0
7910 LET IZ=0
7920 LET IA=0
7930 LET IB=0
7940 LET IC=0
7950 LET ID=0
7960 LET IE=0
7970 LET IF=0
7980 LET IG=0
7990 LET IH=0
8000 LET II=0
8010 LET IJ=0
8020 LET IK=0
8030 LET IL=0
8040 LET IM=0
8050 LET IN=0
8060 LET IO=0
8070 LET IP=0
8080 LET IQ=0
8090 LET IR=0
8100 LET IS=0
8110 LET IT=0
8120 LET IU=0
8130 LET IV=0
8140 LET IW=0
8150 LET IX=0
8160 LET IY=0
8170 LET IZ=0
8180 LET IA=0
8190 LET IB=0
8200 LET IC=0
8210 LET ID=0
8220 LET IE=0
8230 LET IF=0
8240 LET IG=0
8250 LET IH=0
8260 LET II=0
8270 LET IJ=0
8280 LET IK=0
8290 LET IL=0
8300 LET IM=0
8310 LET IN=0
8320 LET IO=0
8330 LET IP=0
8340 LET IQ=0
8350 LET IR=0
8360 LET IS=0
8370 LET IT=0
8380 LET IU=0
8390 LET IV=0
8400 LET IW=0
8410 LET IX=0
8420 LET IY=0
8430 LET IZ=0
8440 LET IA=0
8450 LET IB=0
8460 LET IC=0
8470 LET ID=0
8480 LET IE=0
8490 LET IF=0
8500 LET IG=0
8510 LET IH=0
8520 LET II=0
8530 LET IJ=0
8540 LET IK=0
8550 LET IL=0
8560 LET IM=0
8570 LET IN=0
8580 LET IO=0
8590 LET IP=0
8600 LET IQ=0
8610 LET IR=0
8620 LET IS=0
8630 LET IT=0
8640 LET IU=0
8650 LET IV=0
8660 LET IW=0
8670 LET IX=0
8680 LET IY=0
8690 LET IZ=0
8700 LET IA=0
8710 LET IB=0
8720 LET IC=0
8730 LET ID=0
8740 LET IE=0
8750 LET IF=0
8760 LET IG=0
8770 LET IH=0
8780 LET II=0
8790 LET IJ=0
8800 LET IK=0
8810 LET IL=0
8820 LET IM=0
8830 LET IN=0
8840 LET IO=0
8850 LET IP=0
8860 LET IQ=0
8870 LET IR=0
8880 LET IS=0
8890 LET IT=0
8900 LET IU=0
8910 LET IV=0
8920 LET IW=0
8930 LET IX=0
8940 LET IY=0
8950 LET IZ=0
8960 LET IA=0
8970 LET IB=0
8980 LET IC=0
8990 LET ID=0
9000 LET IE=0
9010 LET IF=0
9020 LET IG=0
9030 LET IH=0
9040 LET II=0
9050 LET IJ=0
9060 LET IK=0
9070 LET IL=0
9080 LET IM=0
9090 LET IN=0
9100 LET IO=0
9110 LET IP=0
9120 LET IQ=0
9130 LET IR=0
9140 LET IS=0
9150 LET IT=0
9160 LET IU=0
9170 LET IV=0
9180 LET IW=0
9190 LET IX=0
9200 LET IY=0
9210 LET IZ=0
9220 LET IA=0
9230 LET IB=0
9240 LET IC=0
9250 LET ID=0
9260 LET IE=0
9270 LET IF=0
9280 LET IG=0
9290 LET IH=0
9300 LET II=0
9310 LET IJ=0
9320 LET IK=0
9330 LET IL=0
9340 LET IM=0
9350 LET IN=0
9360 LET IO=0
9370 LET IP=0
9380 LET IQ=0
9390 LET IR=0
9400 LET IS=0
9410 LET IT=0
9420 LET IU=0
9430 LET IV=0
9440 LET IW=0
9450 LET IX=0
9460 LET IY=0
9470 LET IZ=0
9480 LET IA=0
9490 LET IB=0
9500 LET IC=0
9510 LET ID=0
9520 LET IE=0
9530 LET IF=0
9540 LET IG=0
9550 LET IH=0
9560 LET II=0
9570 LET IJ=0
9580 LET IK=0
9590 LET IL=0
9600 LET IM=0
9610 LET IN=0
9620 LET IO=0
9630 LET IP=0
9640 LET IQ=0
9650 LET IR=0
9660 LET IS=0
9670 LET IT=0
9680 LET IU=0
9690 LET IV=0
9700 LET IW=0
9710 LET IX=0
9720 LET IY=0
9730 LET IZ=0
9740 LET IA=0
9750 LET IB=0
9760 LET IC=0
9770 LET ID=0
9780 LET IE=0
9790 LET IF=0
9800 LET IG=0
9810 LET IH=0
9820 LET II=0
9830 LET IJ=0
9840 LET IK=0
9850 LET IL=0
9860 LET IM=0
9870 LET IN=0
9880 LET IO=0
9890 LET IP=0
9900 LET IQ=0
9910 LET IR=0
9920 LET IS=0
9930 LET IT=0
9940 LET IU=0
9950 LET IV=0
9960 LET IW=0
9970 LET IX=0
9980 LET IY=0
9990 LET IZ=0

```

```

610 LET RA=HR
620 LET CA=HC
630 LET D=2*INT (RAD*2)-1
640 IF F THEN LET RA=HR+D
650 IF NOT F THEN LET CA=HC+D
660 LET F=NOT F
670 GOTO 680
680 PRINT AT RA,HC;CHR# 0
690 PRINT AT RA,CA;CHR# 134
700 LET HR=RA
710 LET HC=CA
720 IF CO=CA AND RO=RA THEN GOT
0 800
730 GOTO 880
740 CLS
750 IF S>H3 THEN LET H3=S
760 FOR T=1 TO 50
770 PRINT "YOU DID IT."
780 NEXT T
790 CLS
800 PRINT "YOUR SCORE IS";S;"."
810 GOTO 840
820 CLS
830 PRINT "SORRY YOU WERE CAUGH
T."
840 PRINT "THE HIGH SCORE IS";H
6: "
850 PRINT "PRESS<ENTER>TO PLAY
AGAIN."
860 LET K#=INKEY#
870 IF K#<>CHR# 118 THEN GOTO 8
60
880 GOTO 80
1000 IF DE(P1)="," THEN GOTO 103
0
1010 LET P1=P1+1
1020 GOTO 1000
1030 LET N3=DE(P2 TO P1-1)
1040 LET P1=P1+1
1050 LET P2=P1
1060 RETURN

```

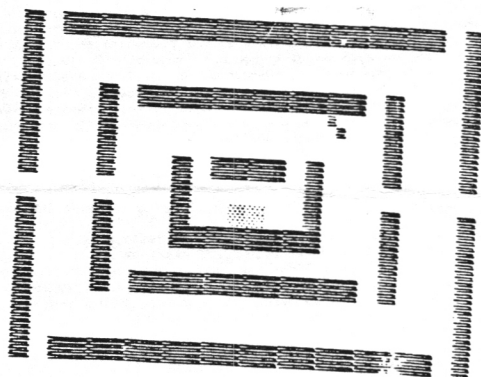

WE HAVE SPECTRUM ROM'S

AVAILABLE TO LIST MEMBERS \$18.00,
Non-members \$19.95. PRICE INCLUDES
POSTAGE AND PACKING. MAIL CHECK,
MO TO

LIST ASSOCIATES
10 Idle Day Drive
Centerport, N.Y. 11721

ITEM: GAME CHANGER INTERFACE
 PURPOSE: CHANGE ATARI GAMES
 SYSTEM: 8K ROM/2K RAM & ATARI 2600
 FROM: HURON VALLEY RESEARCH INC.
 PO BOX 732
 HIGHLAND, MICHIGAN 48031
 PRICE: \$125.00 + \$5.00 S&H

Clever hardware construction, both mechanical and electronic, and a solid comprehension of both 6502 (the ATARI 2600's CPU) and 280 (TIMEX) programming are combined to produce the very powerful "Game Changer Interface". The unit cross-connects your 2600 VCS (Video Computer System) and TS 1000, allowing either one to take control of whole blocks of shared memory. That "shared" memory includes the ROM inside any ATARI game cartridge and "shadow" copies of that ROM in your TS 1000's RAM. With this system you can download the ROM game to your ZX/TS, disassemble the machine code (6502), make game variations or even create your own game from scratch, and then upload your version back to the 2600 for play.

The system consists of two double-sided, plated-through open boards, professionally constructed. The larger, or mother, board plugs into the back of your unexpanded ZX/TS and connects via ribbon cable to the smaller VCS adaptor board. This latter has male and female edge connectors. One inserts into the cartridge slot in your VCS, while game cartridges can be installed in the other.

The mother-board contains 4 HM 6116's (2K Static RAM), and uses some ingenious coding to remap internal RAM above that 8K, for a total of 10K RAM (12K with an extra chip and some soldering). The 4K above RAMTOP contain the actual ROM of the game cartridge. For any size cartridge, the game information is transferred to a long 8 ROM statement for storage. Cartridges over 4K are handled using a bank switching technique like ATARI's. Game execution is accomplished by transferring the game data to the actual bottom of RAM using menu driven software and then placing the TS 1000 in a bus requested mode when power is applied to the 2600.

The smaller cartridge adapter board uses the strength of the fiberglass board to open the VCS and cartridge door slots, and has an on-off switch to allow insertion and removal of cartridges while the system is on.

Menu driven software is supplied on cassette. It includes 2 programs of BASIC and ML which are required to download the cartridges, one for 2-4K games and one for 8K. The 8K game actually works for any size game, but takes longer to SAVE and LOAD, a bother if your actual cartridge is a short one. The third program is called "Change" and that's exactly what it does. A simple 6502 disassembler and monitor are included in this program. They allow you to review the code and change it at will. This is a very nice feature for those shoot-em-up games where you wish you had "just one more ship".

The system works very well and even comes with high quality RF cables and 3 way switch box for your TV set. You need that switch box, unless you use two sets, to switch back and forth between what your VCS and TS are putting out on channel 3 (or 2). I installed an extra 2K RAM chip as insurance for my disk drives data transfer buffer and found the system 100% compatible with AERCO's disk drive. With that system combination I can download, save or retrieve any program in seconds. The question of speed though, does lead us to the few negative aspects of the system.

8K cartridges download into what, in effect, are 10K BASIC programs, and we all know how long they take to load from tape. After you modify, or make your new game, you may want to have an EPROM burned. Also, as the system uses BUSREQ you'll have trouble using the dynamic RAM's (e.g., as in a 16K RAMPACK) in other system expansions. Hunter's board, populated with 6116's, should work, if your decoding is complete.

I had very little trouble loading the programs. The menus are simple and the documentation is spartan. That documentation consists of 7 photocopied typewritten sheets. It includes an installation sketch and hand drawn schematic, essential memory map locations and operating instructions. Perhaps the only flaw in an otherwise superb system, the documentation is brief, and has a number of typos, though none are serious.

Huron Valley promises to dress up the paperwork to match the quality of the rest of their system and to produce a "Tutorial" (sic) newsletter for owners. Adapters to allow use of the system on 1500's and 2068's are also in the works. Overall, while less than perfect documentation usually causes a severe downgrade, I must rate the "Game Changer" highly. It is exceptionally powerful and well designed, and could provide the ultimate in inexpensive game play and design system for a total investment of less than \$175 (including a TS 1000). Overall rating is a 9 out of 10 and would be higher at a slightly lower price.

One final note about Huron Valley, they are exceptionally helpful and courteous on the phone (the owner's home phone number is supplied), and must be rated one of the supportive vendors I've met.

©Copyright 1984
 P.J. Donnelly

Marty J., has been entering some Microsoft BASIC programs into his 2068. He offers the following sample correlation for STRING handling.

MISCROSOFT	RESULTS	SINCLAIR BASIC
MID\$(A\$,3,2,)	LL	AS(3 TO 4)
LEFT\$(A\$,2)	HE	AS(to 2)
RIGHT\$(A\$,2)	LO	AS(LEN(A\$)-1 To)

ITEM: DK TRONICS KEYBOARD
 FROM: DK TRONICS, SUFFERN -WALDEN, ENGLAND (799-26350)
 PRICE: \$72.00 + S&H (Depends on exchange rate)

About a month after my second order (the first bounced because of some problems with VISA), I received my DK Tronics "big" keyboard for my TS/1000.



The keyboard case is made of a soft black plastic and has 40 grey keys and an additional 12 red keypad keys. The feel of the keys is good and clear vinyl markers on each key contain the standard Sinclair codes, as used in the U.K. (e.g., NEWLINE for ENTER). Inside the case is DK's "motherboard" which is simply an extension of the ZX81 buss to the rear of the case, but which has an extra male connector sticking up. This extra connector allows you to securely mount any one peripheral inside the case. The usual choice, and mine, is to install a 16K memory pack in this area. This leaves the newly exposed rear connector available for other devices. DK also provides enough room for small internal power supply for graphics ROM assembly. The standard phone plug connectors are exposed through a slot in the back of the case.

Assembling the DK Tronics keyboard was easy for the most part. Standard installation requires only that the DK keyboard and ZX81 have the screws holding them together removed and the ZX81 P.C. board placed inside the keyboard case. The ZX board plugs in to the motherboard via the edge connector. Two specially prepared connectors then simply plug into the keyboard slots. There is one problem with the standard installation however. The DK product is intended for use with a UHF modulator. These come out of the case about 1 1/2" further from the back than the USA's VHF output and an extra 1/2" hole has to be drilled in the case. This is no a problem, as the material is very soft and easier to work than wood.

The workmanship on the board I received was not very good. I had to realign the motherboard and found some of the wooden mounting blocks somewhat off center, as well. Also, DK made no provision for the Ch2 - Ch3 switch in the bottom of the case. Finally, an obvious mold flaw mars the finish on top of my unit.

Other shortcomings include the lack of a space bar, the use of a wooden bottom plate and the total lack of shielding (not required in the UK, I'd guess). These shortcomings are offset somewhat by the fine "feel" of the keyboard, the ease with which the plastic material can be worked, the reasonable price and the extra numeric keyboard. On balance, I would rate the DK's keyboard a reasonable value for the money, but recommend you be prepared to use simple hand tools (screwdriver, hand brace, pliers) to "finish" your keyboard. I expect a warranty claim would be tough to follow up. Do ask for the Overseas price, not the U.K. domestic price.

Drill for US TV

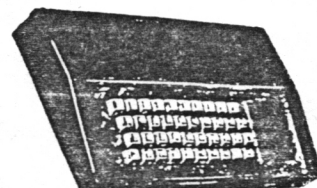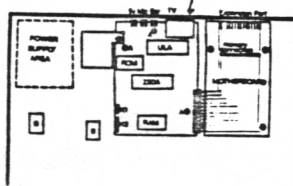

MICROSOFT BASIC

```
10 A$="HELLO"
20 LPRINT MID$(A$,3,2)
30 LPRINT LEFT$(A$,2)
40 LPRINT RIGHT$(A$,2)
```

LL
 HE
 LO

(10774)

SINCLAIR BASIC

```
10 LET A$="hello"
20 PRINT A$(TO 2)
30 PRINT A$(3 TO 4)
40 PRINT A$(LEN A$-1 TO )
```

he
 LL
 LO

NOTE: Lines 20 & 30 are reversed.

5-84

LISTING

TO:

LIST
P.O. BOX 438
CENTERPORT, N.Y. 11721-0438

LIST
P.O. BOX 438
CENTERPORT, N.Y. 11721-0438

22

TO:

The other two lines provided by the printer interface are STB and ACK (strobe and acknowledge). I used the interface with a Centronics 101 printer and Ener-Z says it works with EPSON and should work with most other Centronic style printers. I agree, but suggest you include your printer type in any correspondence you have with Ener-Z.

After getting my R.G. board, I put it through its paces, on and off, for over a month. The RTC lost only a few seconds, and I hooked up switches (Joystick actually) to the input ports. I've used the output ports, all eight lines, with two off-board chips to drive a 3 digit 7 segment display. This last lets me see measurement status without turning on my TV. The A/D converter measured some resistance circuits I'd set up quite accurately and I've even tied it into a thermistor and gotten a fairly good thermometer, accurate without amplification to about 2-3°F. To get the printer interface working, you'll need to make up your own cable. You can get everything you'll need at Radio Shack or a number of the mail order houses. Try to keep your cable under 8-10 feet in length.

If the R.G. board sounds pretty good up to this point, make no mistake, it is. However, it seems that nothing is ever absolutely perfect and there are some negative aspects to the board. Minor turn offs which don't really affect the boards performance included a loose battery connector on my board, some "afterthought" pull up resistors tacked on to assure TTL-CMOS compatibility and the lack of a case. Three more meaningful items, which might even affect your decision to get an R.G. board, do need mentioning. First, is the somewhat hastily prepared documentation. While there is an excellently documented source listing for the EPROM, the supporting narrative on BASIC applications has quite a number of typos and no page numbers. The 29 page documentation swings back and forth between the EPROM and RAM based USR calls, and while a mini hex monitor for loading the RAM version (you must enter this by hand) is provided, the code listing is not. I'd suggest that Ener-Z either prepare two separate versions of the documentation or one complete and comprehensive dual purpose version. I think the average user will be able to use the board, but straight BASIC programmers (i.e., who don't use ML and have little hardware knowledge), may find they'll have to make a call or two to Ener-Z for guidance. I found them most helpful on the phone, myself.

The next complaint is one I have voiced before. This is that we're not told explicitly in either advertising or documentation, which port locations are used. In the case of the R.G. board, with a little digging, the source listing

documentation does indicate addresses 01,03,05 and 07. However, a quick look at the board's partial decoding will show you that any odd numbered port below 80H will respond to the I/O calls from EPROM. Keep this in mind if you have other I/O mapped peripherals.

The other significant "flaw" with the R.G. board has to do more with the "nature of the (TIMEX) beast" than with the board itself. As you probably know, the ZX/TS cannot directly address I/O ports. In order to do so then, we must jump to an ML (machine language) I/O routine and this means using FAST mode and consequently lots of blank screen time and "flicker". I probably wouldn't have thought this to be a significant problem if I hadn't seen JK Audio's 310 board. While this board costs about as much as the R.G. and has fewer features as a stand alone board (I/O ports and clock only), it uses memory mapping to accomplish its I/O functions. This means that the JK board can be run completely from BASIC and provide a continuous rock-steady display while performing its I/O function. I don't feel the R.G. board should be downrated on function because of the difference, only that users should be aware of a need for a little more effort required to produce good looking screens with the R.G. board.

To more than make up for these little flaws, the R.G. offers its high reliability, numerous features, low cost and some bonus features not mentioned in its documentation. The board nominally has one 8 bit input and one 8 bit output port. You could conceivably stretch these, with some off-board multiplexing, to 64 each. How? Schmitt conditioning of signals fed to the A/D converter could give you 8 more digital input lines. Also, the printer port has 8 bits, this time with handshaking. There are other such combinations which you could implement with a few IC's to suit your particular application. A final extra bonus is that about 180 bytes of the EPROM are not yet programmed. Using sufficient care, and an EPROM programmer, you could use this area to add your own special USR routine to the board.

On balance, I found the R.G. board an excellent value and perhaps (next to my \$39.95 TIMEX) the most cost effective computer purchase I've made. If you need any two of the board's features, I recommend buying it. I've given this board a hard to get 9.9 on my price-for-value scale. A "10" could be obtained if the unit were also offered as a kit, the RAM driven version was provided on tape, and documentation was cleaned up a little. Ener-Z has done an outstanding job with its first entry into the ZX/TS peripheral market. As a suggestion for further items, some detailed I/O applications (perhaps collected from users) could be provided and even hardware (e.g., temp probes, light pens, synthesizers) described or made available.

HARDWARE REVIEW

ITEM: REPORT GENERATOR BOARD
 FROM: ENER-Z COMPANY
 PO BOX 635
 FORT WASHINGTON, PA 19034
 FEATURES: RTC, A/D, I/O PORTS, PRINTER INTERFACE
 PRICE: \$89.95 + PH - *Kit Assembly*

Everything Interface

If you could buy only one peripheral which would let your ZX/TS communicate with the real world, Ener-Z's Report Generator just might be it. The board's features include a real time clock, analog to digital interface, Input/Output ports and a Centronics printer interface. All those features, and the under \$80 price tag, sounded like too good a buy to pass up to me, especially since one or two to these features alone would cost more than this board from most other vendors. Does the R.G. deliver? Let's take a look.

Physically, the R.G. board is 4" X 6" and has a cleanly designed physical layout for its 16 IC's and assorted passive components. Construction is professional, with few jumpers, plated through holes, and sockets for the more critical IC's. An on-board regulator is supplied. This helps to keep your ZX/TS's internal regulator cool. A battery holder is provided for the real time clock (RTC) and most of the offboard tie-ins can be made using standard DIP (dual-in-line pin) headers. These last are easy to obtain and inexpensive. In most uses, extra ground or 0 volts lines are provided. These fall between the active lines and should help keep down the effect of transients in your ribbon cables to the real world. The board plugs onto the ZX/TS expansion port and a through-edge connector is provided for other add-ons (e.g., RAMPACKS).

The heart of the R.G. board is a Z80 PIO (peripheral input/output) chip. Through the very clever use of an internal data bus (on the R.G. board), Ener-Z has expanded the capabilities of this simple chip to allow it to address what, in effect, are more than five (5) separate port configurations instead of the conventional two (2). Two versions of R.G. are available, one has all its software on a 2716 EPROM (mine is this type), the other has the driver software in RAM. The RAM version is required if you already are making use of the 2800H to 2B00H area where the EPROM version would normally reside. All functions on the R.G. board are made by USR calls to the appropriate subroutines on the EPROM, which, in turn executes the I/O functions.

P.J. Donnelly

An OKI MSM 58321 clock chip provides the year, month, day, week, hour, minutes and seconds for the RTC. With 3 Nicad batteries installed and the clock setting software (supplied as a listing) entered, you need only enter the correct time once and your ZX/TS will always know exactly what time it is. This is especially helpful if you want your ZX/TS to perform certain I/O functions at specified times.

Eight bit input and output ports are provided by a 74LS 244 buffer and 74LS 373 latch respectively. The inputs can monitor digital signals in the TTL range (0 or 5 volts). Real world signals can either be directly coupled to the buffer lines (e.g., simple switches) or coupled through conditioning circuits (e.g., relays). Outputs are also TTL compatible, through load carrying capacity is only moderate. To drive a large fanout or heavy load, you'd need a power amplifying/buffering stage (e.g., triac to run 110 volt circuits).

The analog converter section of the board uses a National ADC0809, eight bit, eight channel port to convert real world signals in the range of 0-5 volts into their digital equivalents. As an example, a measurement of about 50 means the ADC input is seeing about 1 volt d.c. With eight channels, you can monitor the status of 8 separate analogue devices. Typical uses here include monitoring rotary type joysticks (paddles), thermistors, photo-voltaic cells, peak detector circuits and pressure transducers.




Up to this point we've seen how this board can tell what is happening off-board (input and A/D), know when it's happening (RTC) and even perhaps do something about what it sees (output). Now we're at the stage where, perhaps, you can see how the board got its name. The unit can also generate reports about what's going on, this time by using its final feature, a Centronics parallel printer interface. For this important, high speed task the PIO ports are used directly. Eight data lines transmit ASC II character codes generated by a lookup table in the EPROM. The EPROM effectively "overlays" the Sinclair ROM for this operation, allowing the support of Sinclair's LPRINT, LCOPY AND LLIST commands directly, for the printing of the standard character set. Graphics are not directly supported, but special USR calls can produce a byte code which will produce other characters depending on your printer's capabilities. The overlay of Sinclair's ROM appears to be done with a tricky application of the ROMCS signal when the printer commands are invoked.

Carefully insert the ROM board assembly into the vacant ROM socket (U16) of the T/S 2068.
 Dress the wires from the toggle switch into the computer cartridge section to avoid a possible short circuit.
 Replace the top of the computer case. Do not replace the screws at this time.
 Connect the power cable and video cable into the computer.
 Apply power to your TV and activate the computer switch "ON".
 If all is well, the copywrite message will appear on the TV screen.
 If vertical lines appear on the screen, turn the computer off, flip the toggle switch to the opposite position and activate the computer switch again.
 If everything is OK, turn off computer power, raise the top of the computer case and insert the other ROM IC into the vacant socket on the ROM board.
 Drill a hole in the back of the computer case and install the toggle switch.
 Reassemble the computer case with all hardware.
 Flip the toggle switch to the opposite position and activate the power switch on the computer.
 The copywrite(s) should appear on the screen on your monitor.

Parts required: 1 each unless otherwise noted

Conductive foam pad.....Radio Shack 276-2400
 Multi-Purpose Plug-In Breadboard.....Radio Shack 276-155
 Low Profile 28 pin IC socket.....Radio Shack 276-1997
 Wire Wrap Wire.....Radio Shack 276-501
 .01 Disc Cap.....Radio Shack 272-131
 2- 4.7K - 10K, 1/4 W resistors.....Radio Shack 271-1335
 Sub Mini Toggle Switch SPDT.....Radio Shack 275-326
 Wire Wrap socket, 3 level..DIGI-KEY, Highway 32 South, PO box 677, Thief River Falls, MN 56701

Happy Soldering.....Bob Gilder

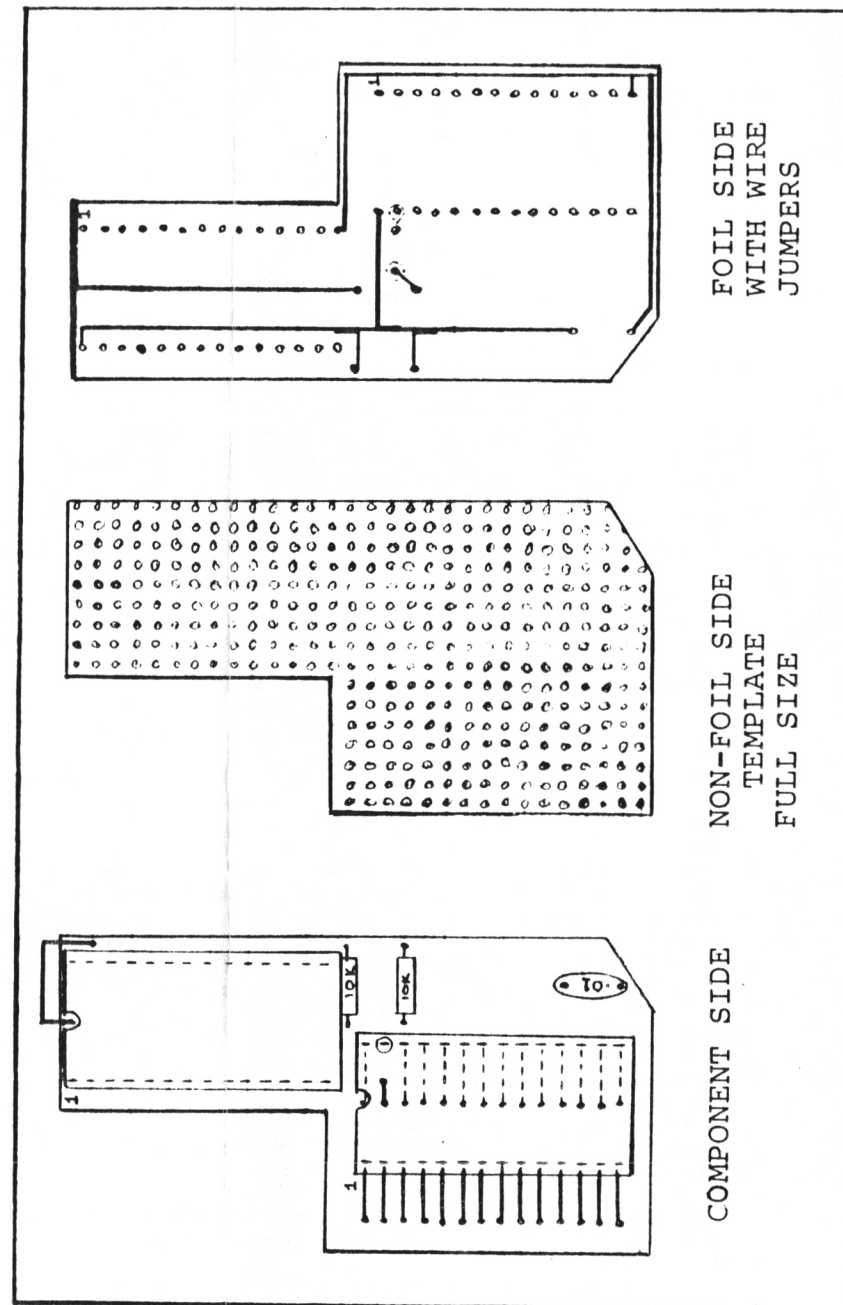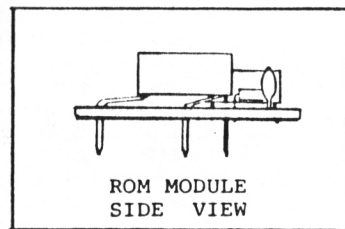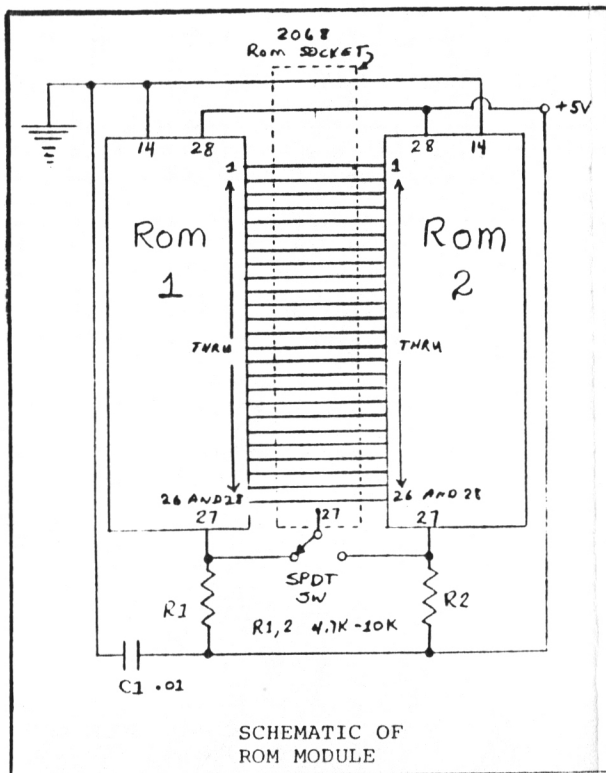

LIST GROUP

PII

11/84

The following instructions for building a switchable ROM Module are for those individuals who are experienced at scratch building electronic projects. I have built 3 modules. Each one has operated with out a problem. If you decide to build a Module and cannot get it to operate properly, contact me in care of L.I.S.T. and I will do my best to try to assist. Lets get to it.

Open the computer case using instructions from last month's issue of L.I.S.T. and carefully remove the ROM (U16) from the socket. Place the ROM in foil or conductive foam. Using the full size template provided, cut the PC grid board to size. Smooth all edges with a fine file.

Next step is to prepare a 28 pin, 3 level wire wrap socket into an offset socket.

Cut a small scrap of perforated PC board with 7 rows of holes. Row 1 and row 7 must be cut along the perforations, leaving 5 rows of holes. This will become a lead bending jig.

Hold the 28 pin W/W socket with pin 1 facing away from you and to the left and all leads (pins) facing down.

Carefully bend pins 2 through 13 upwards and to the left.

Turn the socket over and place the lead bending jig, center row of holes over pins 1 and 14 and hold firm against the socket body.

Bend pins 2 through 13 upwards, aligning each pin along the perforated edge of the jig. Remove the jig and bend pins 1 and 14 down (as pins 2 through 13 were previously bent).

Lay the jig against pins 2 through 13, holding the jig firmly against the socket and bend up pins 1 and 14.

The remaining row of pins must be bent in the same direction as pins 1 through 14, however pins 27 and 15 must be used to secure the jig.

NOTE: Pin 27 MUST NOT BE BENT TO FORM AN "L". Pin 27 is used as a control select line for one of the ROMs.

Repeat the previous steps and bend pins 28, 26 through 15 to form an "L".

If the socket pins look a little irregular as to alignment, do not worry. Trial fit the socket into the PC board.

If a vise is available, place a small piece of wood between both rows of pins (bottom of PC board) and a thin section of scrap wood over the top of the socket and place in the vise. Slowly and carefully close the vise until the socket body is approximately 1/16" from the PC board.

Remove the assembly from the vise and straighten each of the 27 pins with a needle nose pliers.

Place a pencil mark at the location of missing pin 27 of the double row of pins; then remove the socket from the PC board.

Insert a stiff piece of wire (or a spare wire wrap pin) in the hole in the PC board previously marked with a pencil at pin location # 27. Bend the end of this pin to half loop (non copper side of PC board). The end of the loop should protrude through the PC board at a hole next to the pin. Solder in place.

Insert the wire wrap socket into each of its 28 respective holes on the PC board.

When satisfied with the socket pin alignment, solder each of the 28 pins to the PC board.

Using a small fine tooth file, shape the inner and outer edges of the double row of socket pins to a chisel edge.

Carefully plug the PC assembly into the vacant ROM socket (U16) to insure clearance between the ROM board and the computer sub-assembly board. Remove the ROM board and file any areas required for additional clearance between both assemblies.

Place the low profile 28 pin socket into appropriate holes on the ROM board with pin 1 (or notch) on socket facing in the same direction as the wire wrap socket and solder in place.

Using the component side diagram, insert the .01mf capacitor into the PC board and bend both leads to secure in place.

Preform the leads on both 10K resistors and insert into the PC board and bend the leads to secure in place.

Strip the insulation from a 6" length of wire wrap wire and connect to pin 28 on one IC socket. Dress the wire along the bottom of the PC board and connect to pin 28 of the other IC socket. Solder both joints. This is the +5 volt bus.

Repeat the previous step, interconnecting pins 14 on both IC sockets. Solder both joints. This is the ground bus.

Bend the leads from the .01mf capacitor and connect one lead to the ground bus and the other lead to the +5 volt bus, then solder both connections.

Connect one lead from each 10K resistor to the +5 volt bus and solder these connections.

Connect and solder a short length of w/w wire to the free end of the 10K resistor closest to the low profile IC socket and connect and solder the other end of the wire to pin 27 on the low profile IC socket.

Connect the free end of the second 10K resistor to the straight through pin (27) on the wire wrap socket and solder in place.

Solder a short length of wire to pin 27 of the double row of pins. This is the single pin soldered in place earlier. Solder the other end of this wire to a pad close to both 10K resistor leads which connect to pins 27 on both IC sockets.

Take a break and carefully inspect all soldered connections for shorts and/or unsoldered joints.

Using wire wrap wire, interconnect pins 1 through 13 and 15 through 26 on both IC sockets, then solder in place. TAKE YOUR TIME and be careful not to create any solder bridges between socket pins. (Pin 1 on one socket connects to pin 1 on the other socket.....and so on).



Connect and solder an 8" length of wire at the junction of one 10K resistor and pin 27 of an IC socket.

Repeat previous step for the other 10K resistor/pin 27 junction. Solder the free ends of the wires to the outside pins on the SPDT toggle switch. One wire to the N/O pin, the other to the N/C pin.

Connect and solder an 8" length of wire to the solder pad with a wire connecting to pin 27 of the double row of pins. Connect and solder the other end of this wire to the center pin on the switch.

Again, INSPECT ALL solder joints for any shorts. Use an ohm meter to check continuity of all parallel joints and between all socket pins.

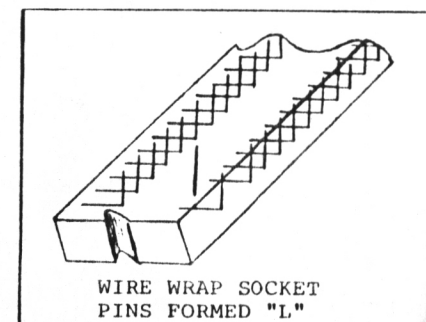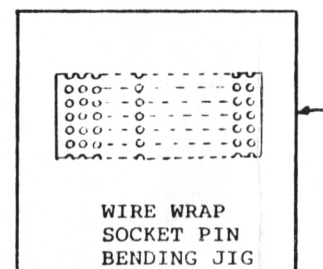If all is OK, insert the ROM board into a conductive foam pad. Carefully place one ROM IC only into any one IC socket on the ROM board.



HARDWARE REVIEW

ITEM: EMU-1 SPECTRUM EMULATOR
 FROM: DOUG DEWEY (ENTER LENGUA)
 206 JAMES STREET
 CARRBORO, N.C. 27510
 FUNCTION: CONVERTS YOUR 2068 INTO A SPECTRUM
 PRICE: \$60.00 (INCLUDES P&P)

Doug Dewey's EMU-1 is a small (2" X 3"), open, double sided, p.c. board which plugs into the cartridge port of your 2068. It contains a 74LS155 for chip select and a 27128 EPROM, programmed to look like an LROS (Language ROM Oriented Software) package to the 2068. Once recognized by the system, LROS's take over control, and this one is programmed to act just like a Spectrum ROM.

I received my EMU-1 about 1 week ago and taking it out of its foil wrapped box with trembling fingers, inserted it into my 2068's cartridge port. It's a fairly snug fit, and close attention to the attached instruction sheet helps make the operation go smoothly. In addition to the insertion/removal instructions, Mr Dewey provides a 4 page letter describing the background and use of the board, some encouragements and warnings to prospective users.

Once you power up, the 2068 initializes itself and then checks the first few bytes of whatever is in the cartridge port. In this case, it finds there is another "language" you want to use and transfers control to that chip. (You could be running FORTH, for example). What you'll see on the screen at switch on is the familiar double copyright notice. Immediately however, as control is transferred to your "Spectrum" Eprom, the system reinitializes and only the @ 1982 Sinclair Research notice remains. When that happens, you've got yourself a Spectrum.

The board works well with all the Spectrum Software we could dig up (see lists), and since U.K. software sells for about 1/2 of its U.S. equivalent, a whole new world of computer power is available to you. We've even ordered PASCAL, the Hobbit and Jet Set Will, based on the performance of the board.

There are some minor drawbacks to the board of which you should be aware. First, is the fact that its an open board. While this is somewhat objectionable from a cosmetic standpoint, more important is the possibility that you could damage the chips in handling. Take normal precautions to prevent static electricity buildup. Second, the edge connector is not gold plated. This means it can only take a limited (though still perhaps in the hundreds) number of insertions and removals before needing to be re-tinned. Again, you can correct this yourself, by having the edges gold plated. These are, as we said, minor complaints, and should prove to be of little importance to most users.

Finally, you should also be able to LOAD and run your existing library of BASIC programs with very little difficulty. The only commands that cause a problem for the interpreter are ON ERR, STICK, SOUND, and FREE. Peaks, Poke and USR's will work, but perhaps not as you expected, so check these also.

The EMU-1 is perhaps the most powerful add-on you can get for your 2068. With it, you'll have access to a tremendous installed base of UK software and still be able to use your 2068's extra capabilities and U.S. software. I rate the EMU a 9.7 out of 10.

@1984 P.Donnelly

CATALOGS RECEIVED

Integrated Data Systems
 11 Brighton Avenue
 Toronto, Canada M4M 1P3
 (416) 466 5571

Exceptionally Complete Catalogs for the ZX/TS & 2068 - The ZX/TS is 34 pages of full size type with descriptions.

John Oliver
 11601 Whidbey Drive
 Cumberland, In. 46229

For the dedicated hardware enthusiast. Memory, Eprom (read & program) boards and connectors - Bare Boards and parts kits available (see SQ back issues).

BCD Electro
 PO Box 830119
 Richardson, Tx 75083-0119

Disk Drives, Disks power supplies
 Disks at 1.00 each Drives @169.00ea

D. Lipinski Software
 2737 Susquehanna Road
 Roslyn, Pa. 19001

BASIC only home & business
 TS 1000 & 2068

E. Arthur Brown
 3404 Pawnee Drive
 Alexandria, MN, 56308

Hardware & Software
 All at or near full list price.
 Claims availability of Smart 11 software.

Knighted Computers
 707 Highland Street
 Fulton, N.Y. 13069

Most hardware & software
 Somewhat below list prices

P.V. Tubes
 104 Abbey Street
 Accrington BB51EE Lancs

Software (Spectrum)
 and hardware replacement
 parts for ZX81 & Spectrum

Melbourne House
 Castle Yard House
 Castle Yard, Richmond
 TW106TF

Books & Software
 for Spectrum (e.g., ROM
 disassembly

Software Supermarket
 87 Howards Lane
 London, England SW156NU

All Spectrum & ZX81
 titles

POLICY ON CONTRIBUTED MATERIAL:

We are always looking for interesting articles, programs, reviews etc. to help keep our members informed and entertained. Articles submitted for publication are printed on the following basis:

1. You, the writer, maintain the full copyright and can resell, lend or give away your work, as you wish.
2. We are granted the right to publish your material, in the original issue in which it appears. Reprints (e.g., to supply orders for back issues) will include your material as a part of its original issue. We are not allowed to sell your material in any other way, without your express written consent;

We can't (for now) pay you for your material, but you will receive a copy of the issue in which it is published, even if you're not a member. You may get more than one issue and you will definitely earn the respect and appreciation by your grateful peers.

If you have a program or article about something you've tried, please send it in. Our group interests are so varied that I can almost certainly guarantee that someone else can use your expertise to solve his problem.

Doug Dewey's EMU-1 is a convenient and effective way to achieve Spectrum emulation on your TS 2068. It has the distinct advantage of not requiring you to open up your machine and go mucking about inside. There are however, two other ways to provide Spectrum capabilities on your 2068.

1. Disconnect your computer from everything and clear a work space for your labors. Remember to ground yourself well to prevent static electricity from damaging your machine.
2. Turn your 2068 belly-up and loosen the seven Philips head screws (3 large and 4 small).
3. Carefully, holding the sides of the case together, turn the machine back upright. The screws will fall out, if you haven't removed them, so make sure they don't get lost.
4. Place the machine on the table and slowly lift the top cover from the front. There is only one connection between the top (Keyboard) and bottom (circuit board) and that is the keyboard's flat cable. This cable is more durable than the ZX81 version, but is still easily damaged. You can now either prop up the top of the case, or better yet, carefully and slowly pull the flat cable out of its socket. Try to pull it out evenly by grasping it at either side using both hands (while the backs of your hands hold up the top case).
5. With the top removed, look for U16, the 16K ROM. We can ignore the other 8K chip (U20) as it is simply not used by the Spectrum. Using a IC extractor, remove U16. If you don't have an IC extractor, a screwdriver with a large flat, but thin blade and thin shank can be used. Place the tip of the driver between one end of the chip and its socket and twist slightly. When one end of the chip starts to move, go to the other end and repeat the operation. Keep doing this, a little at a time, until the chip is out. Place the chip in the back of the plastic foam pad in which your new Spectrum ROM is still sitting. (This is antistatic foam).
6. Make sure the pins on your new ROM are straight and then insert the chip, starting with one row and then the other into the socket. If the pins seem too wide apart, place the chip on its side on the table and gently roll it into the pins on one side, this should close up the gap, on all pins, slightly. Make sure you put pin 1 of the ROM where it belongs. Pin 1 is in the upper left hand corner of the chip. It is usually marked with a dot. Also the top of the chip will probably have a notch, as shown in the outline on the drawing.

LIST ASSOCIATES
10 IDLE DAY DRIVE
CENTERPORT, N.Y. 11721

-
- The diagram illustrates the internal architecture of the Edge computer. Key components include:
- CPU:** A central processing unit labeled "CPU" at the top center.
 - Memory:** Includes "RAM" modules on the left and "ROM" modules on the right, connected via a bus system.
 - Storage:** Features a floppy disk drive and a hard drive, both connected to the main system bus.
 - Peripherals:** Includes a keyboard controller, mouse controller, and various expansion slots for additional hardware.
 - Power & Cooling:** Shows a power supply unit and several cooling fans for temperature management.
- The diagram uses standard electronic symbols for components like capacitors, resistors, and integrated circuits, along with signal traces indicating data flow between different sections of the board.

T82068 PC BOARD COMPONENT LAYOUT

9/84

There is a comprehensive look at adventure games in the last two chapters which I highly recommend to any serious D & D fans.

I only paid 1/2 price for my copy of the "Pocket Book" and felt it a good bargain at that price. Some other minor faux pas which contributed to downgrading the books value; benchmarks are promised for run times and not given, and 50 cycle references are not corrected to 60 cycles in his clock program.

Overall, I thought the book worth more than I paid for it, but perhaps not worth the list price.

Table 3
JOYSTICK CONNECTOR SIGNAL ASSIGNMENT

PINS	SIGNAL NAME	FUNCTION
1	DIR1	Direction One (active low).
2	DIR2	Direction Two (active low).
3	DIR3	Direction Three (active low).
4	DIR4	Direction Four (active low).
5	-	Not used.
6	BUTTON	Button Input (active low).
7	5V	+5 VOLTS
8	RSTB	Read strobe.
9	-	Not used.

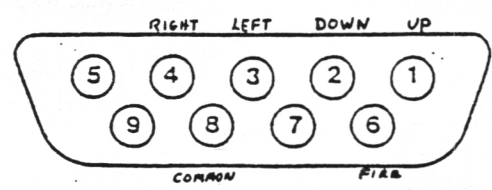


Figure 3 JOYSTICK CONNECTOR

JOYSTICK CONNECTORS

The T/S 2000 has the built-in capability to use two eight-position joysticks. These joysticks are industry-standard. The connectors are industry-standard 9-pin "D" type connectors. The layout of the connector, and the function of each pin is given below in Table 3 and Figure 3.

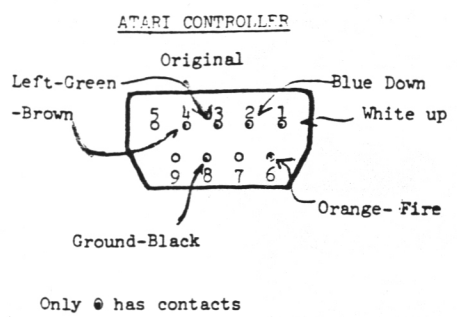


Fig 1(a)

Uses Quik
Connect Terminals
For Edge Connectors

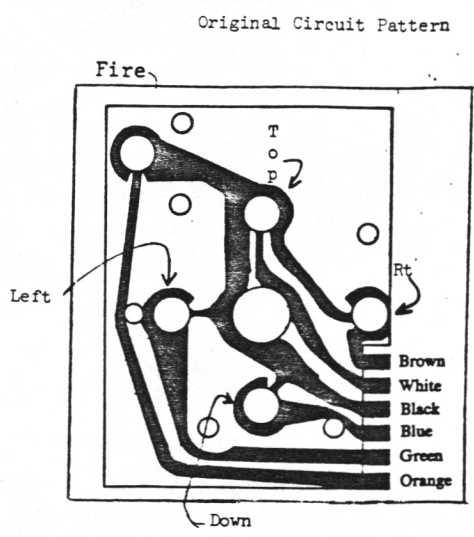


Fig. 1(b)

© 1983
P. Donnelly
101 DE DAY DR
CENTERPORT NY 11721

BOOK REVIEW THE ZX81 Pocket Book

AUTHOR: TREVOR TOMS (1981)
FROM: Reston Publishing Co. Inc.
Reston, Va. (Prentice Hall)
COST: \$10.95

Trevor Toms "Pocket Book" is a handy little compilation of hints and tips for programming your ZX81 - TS/1000. It is 128 pages long and is divided up into 9 easy-to follow chapters. There are practically no typos, which I thought quite unusual until I learned that Mr. Toms used a Panasonic JD800 with Wordstar to compose the text.

As with most other texts of this type, it is assumed you have already read the originally supplied BASIC Manual. The first few chapters begin by presenting in intermediate programming techniques, string searches and handling, efficient programming (conserving memory or increasing speed), "Big" characters, decimal justification and miscellaneous tips. Many of these are quite valuable to readers with the unexpanded ZX/TS computer and most are reasonable well explained. Mr. Toms does tend to carry variables around outside his subroutine listings which is somewhat annoying, but is, after all, the way the computer does it. His "Big" characters program could use somewhat more explanation, but does show two very interesting ways to address the problem. An example of the valuable little tips is the following short program line:

200 PAUSE 4F4


Which can be pronounced "pause Four-ee-Four" and means just that; as 40000 is greater than 32,767 and the computer will wait for a keystroke, "forever".

In chapter 7 we address machine code. Mr. Toms demonstrates the use of REM statements, arrays and the area above RAMTOP for storing machine code. A valuable list of the advantages and disadvantages of each storage area is provided. Of particular interest is his use of "relative" jumps using lines like:

120 GOTO USR X+200

There is an excellent opportunity for implementing READ, DATA and RESTORE through the use this technique, coupled with string slicing, simply by putting your DATA values in REM statements.

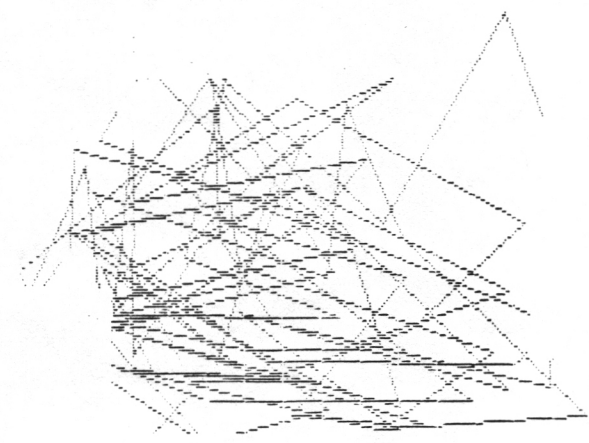A "rather deluxe" monitor is provided. Actually I found it rather "basic". A variable loader program is supplied and this is fairly efficient, but Mr. Toms assumes that his readers know how to change one variable in a list of subscripted variables without rerunning the entire program. I have found this not to be the case with many users.



```

1000  Sx=127  LET Sy=87
1010  PLOT Sx
1020  I=1
1030  X=INT (RND*127)
1040  Y=INT (RND*88)
1050  Z=INT (RND*43)
1060  ((INT (RND*3+.05))>1) THEN
1070  X=(X*(-1))
1080  ((INT (RND*3)>1) THEN
1090  X1=Sx-X
1100  Y1=Sy-Y
1110  X1<=0 OR X1<=0 THEN
1120  Y1<=175 OR Y1<=0 THEN
1130  ((X1+Z1)>=255 OR (X1-Z1)<=0
1140  OR (Y1+Z1)>=175 OR (Y1-Z1)<=0
1150  GO TO 1030
1160  DRAW X1,Y1
1170  LET Sx=X1
1180  LET Sy=Y1
1190  I=I+1
1200  IF I=100 THEN
1210  GOTO 1000
1220  END

```